
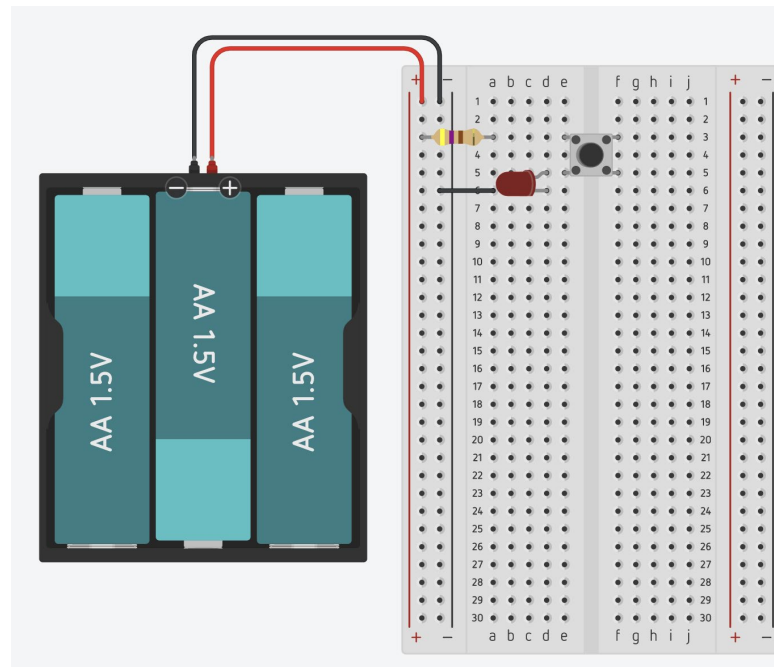


Basic LED Circuit With Button Switch

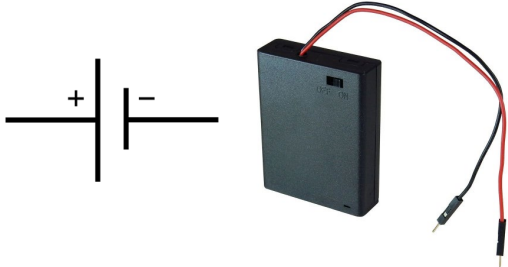

We will be building the Basic LED Circuit with a Switch. Here are the components you will need.


4.5V BATTERY PACK




470Ω RESISTOR




BREADBOARD

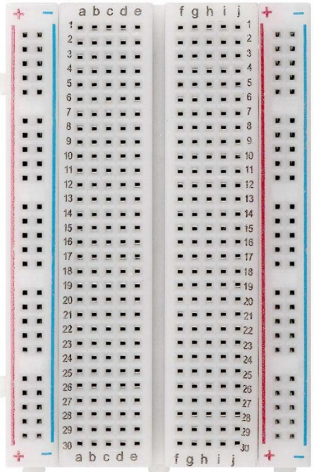

LED (Light Emitting Diode)

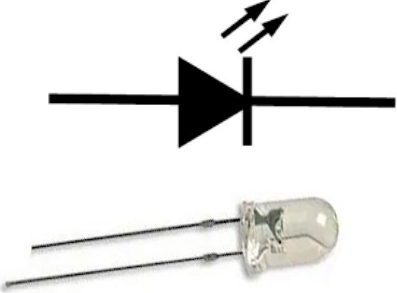

PUSH BUTTON SWITCH

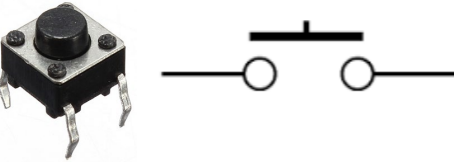

WIRES



Figure A: Circuit Diagram or Schematic



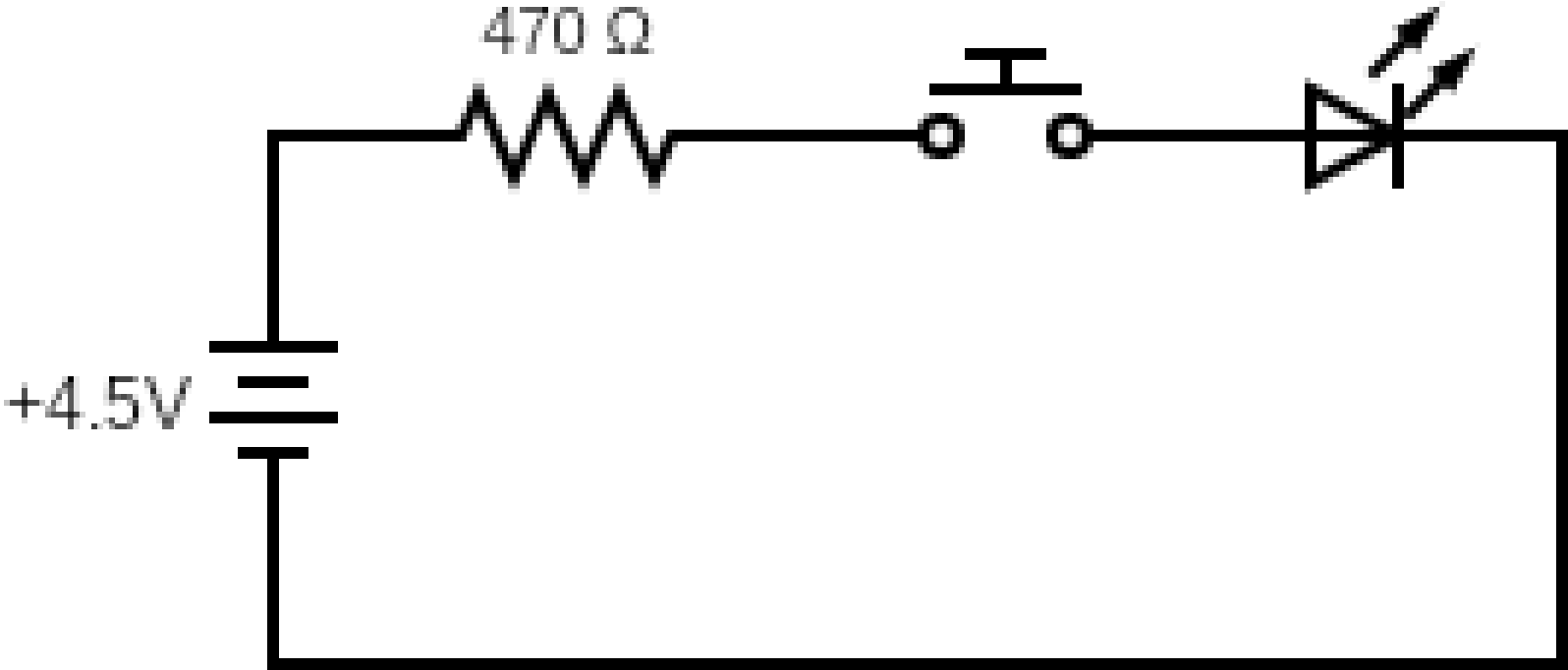




Figure B: Drawing of your circuit

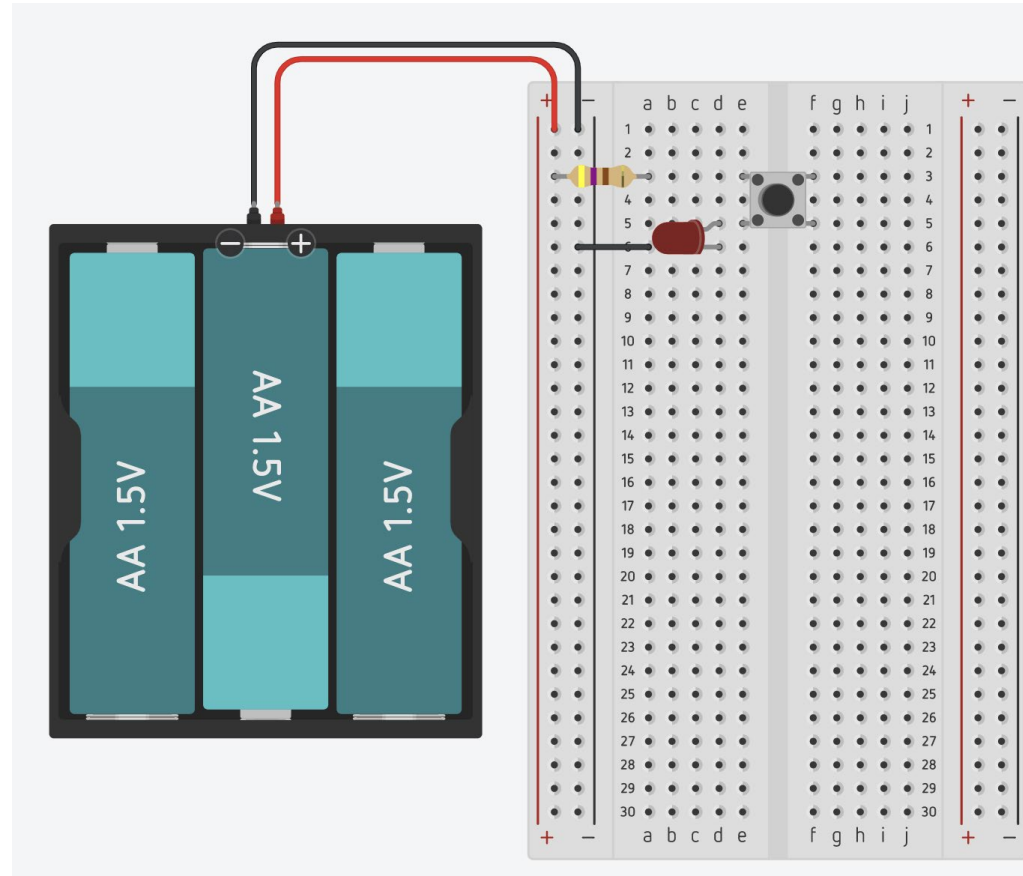


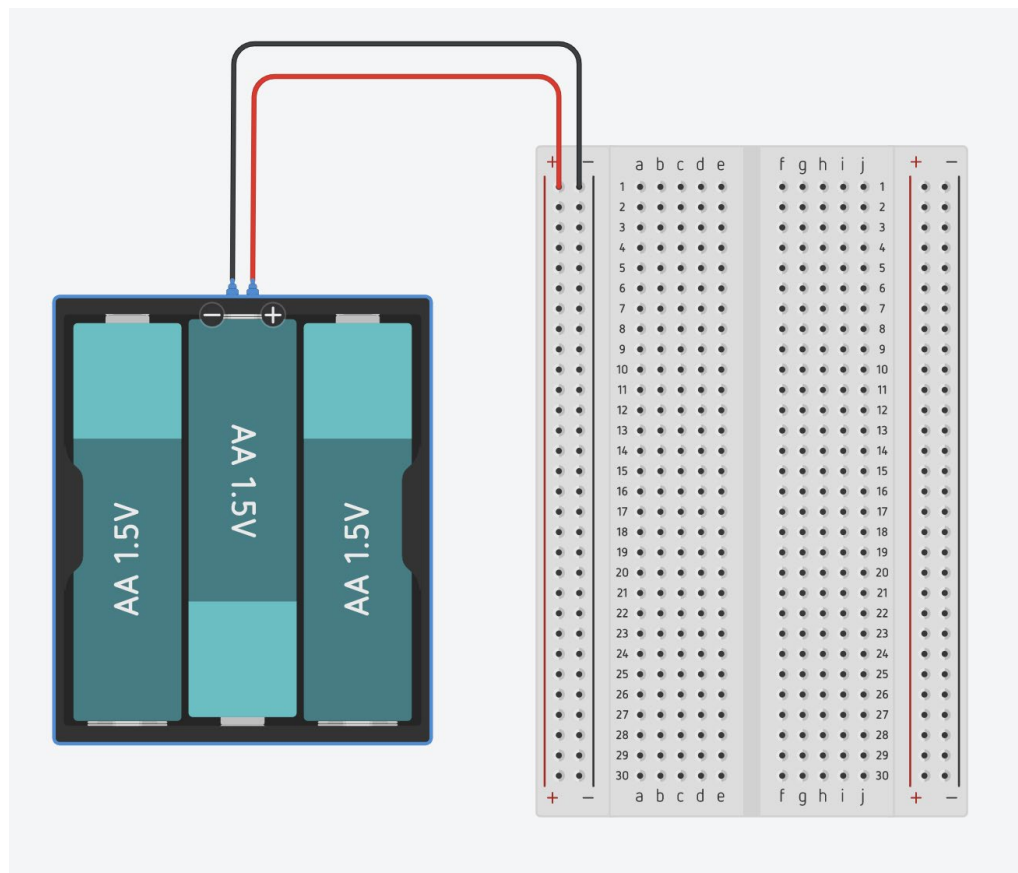
Hook up your 4.5volt battery to the breadboard



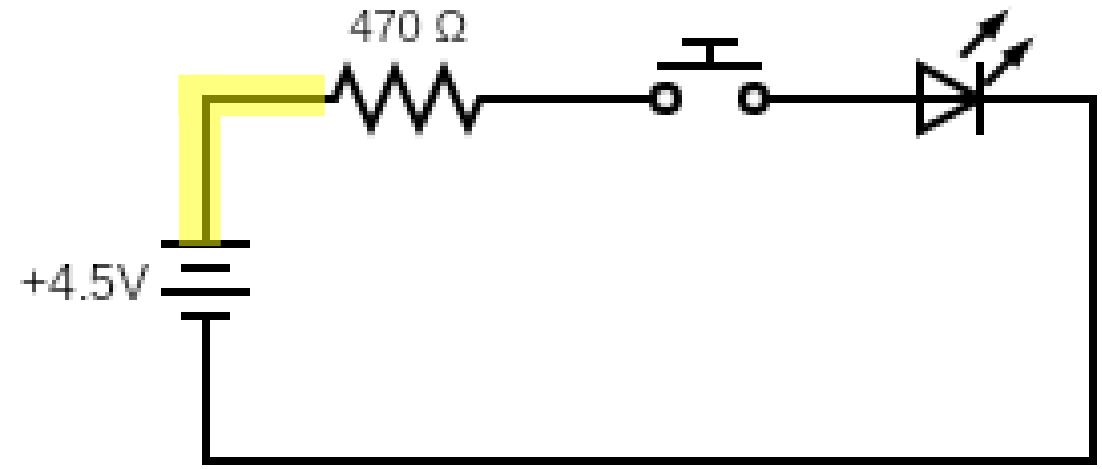
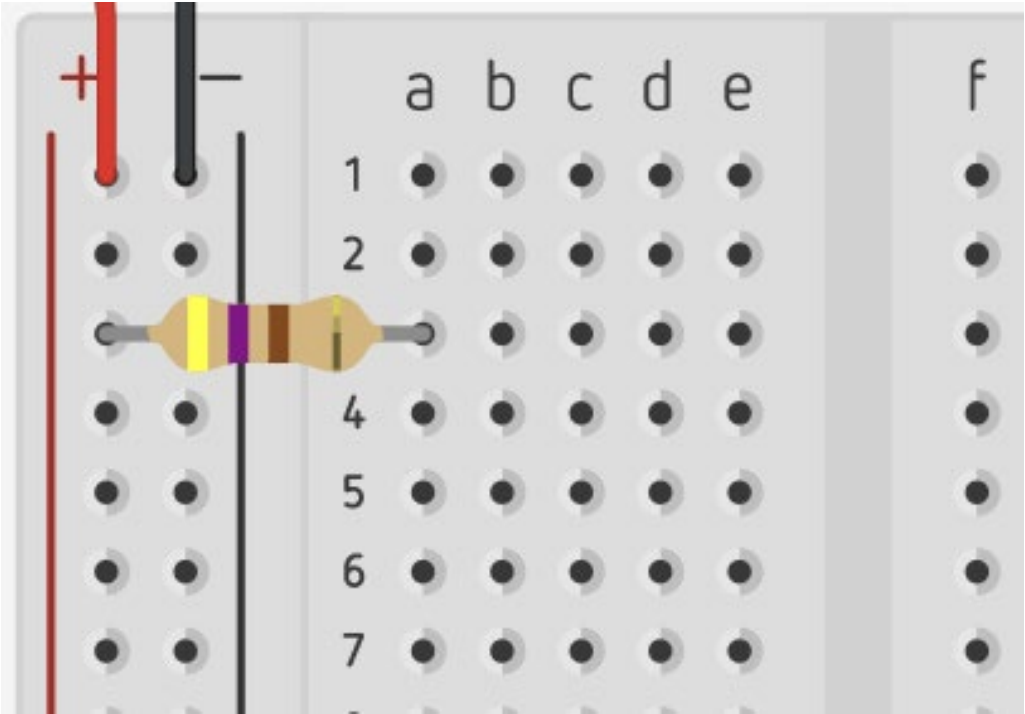
Make sure the positive (+) and negative (-) ends of the battery are connected to the appropriate (+) and (-) power buses on the breadboard. Make sure the battery is turned off! Only turn on the battery after the circuit is completed!



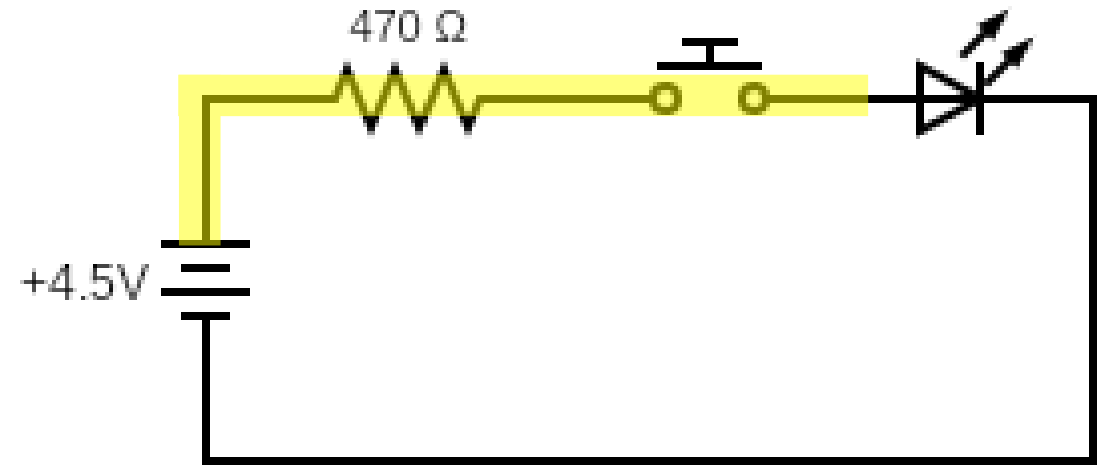
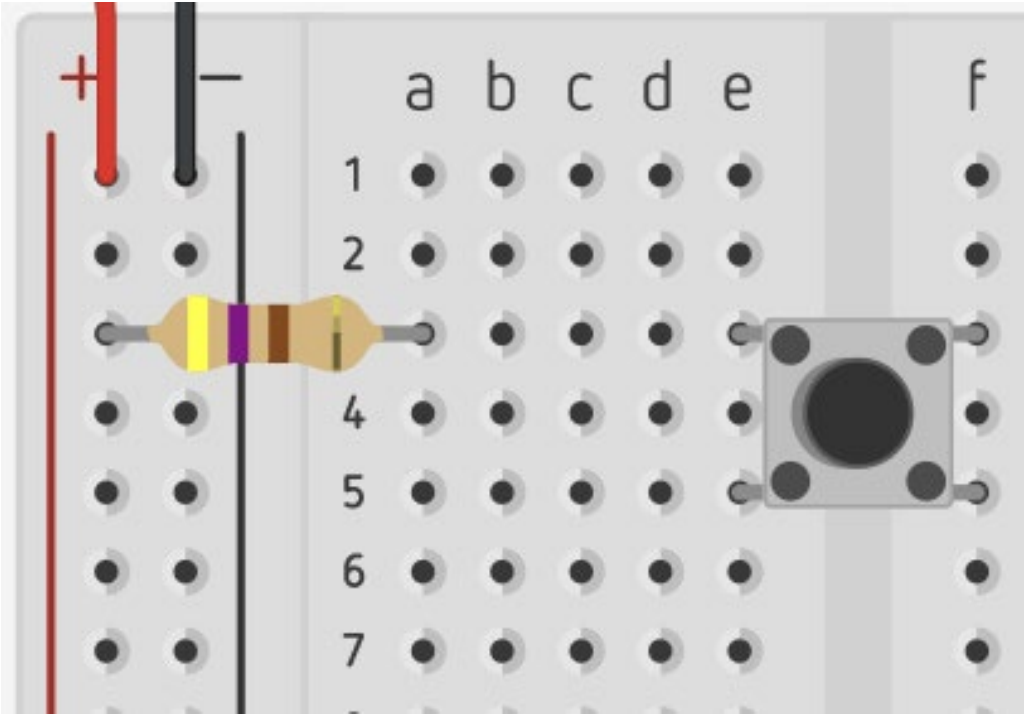
Connect a jumper cable from the (+) power bus to a 3A on the terminal strip.



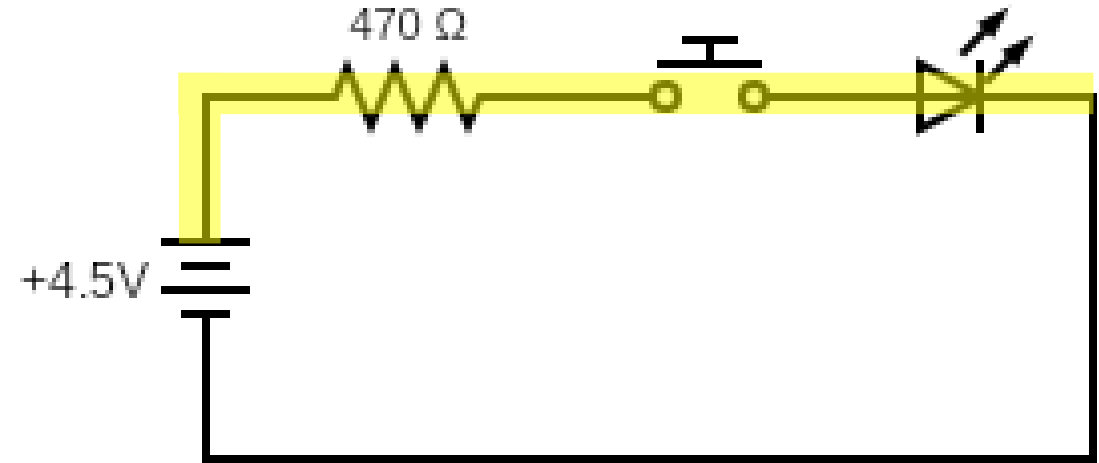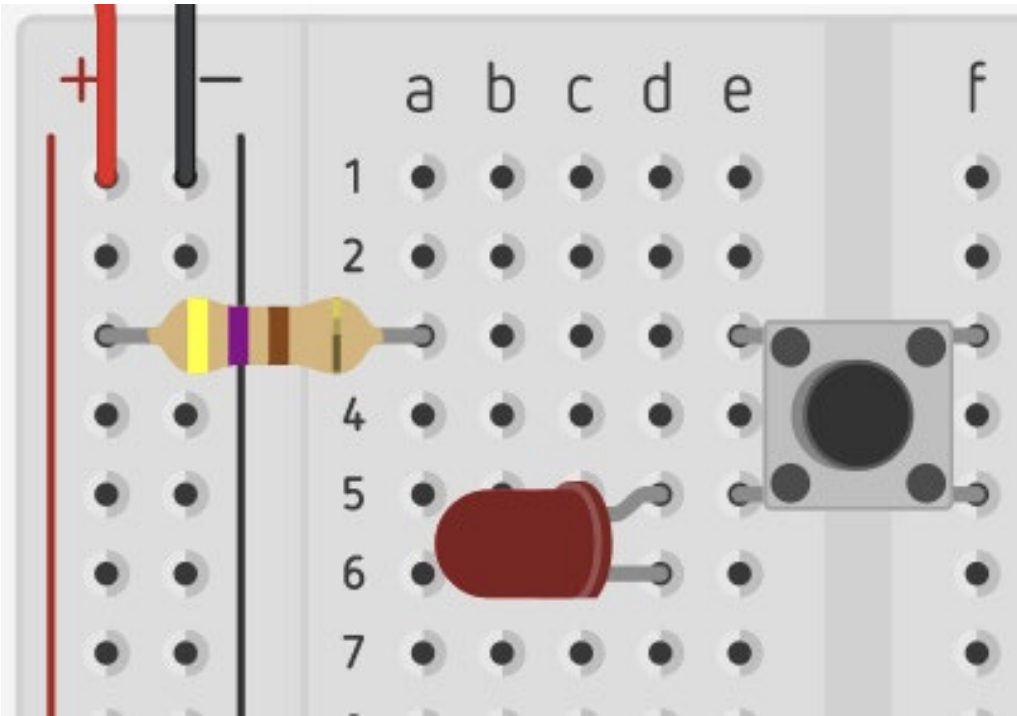Connect your push button switch so that one of the sides pins is in 3E and 5E and the other sides pins are in F3 and F5



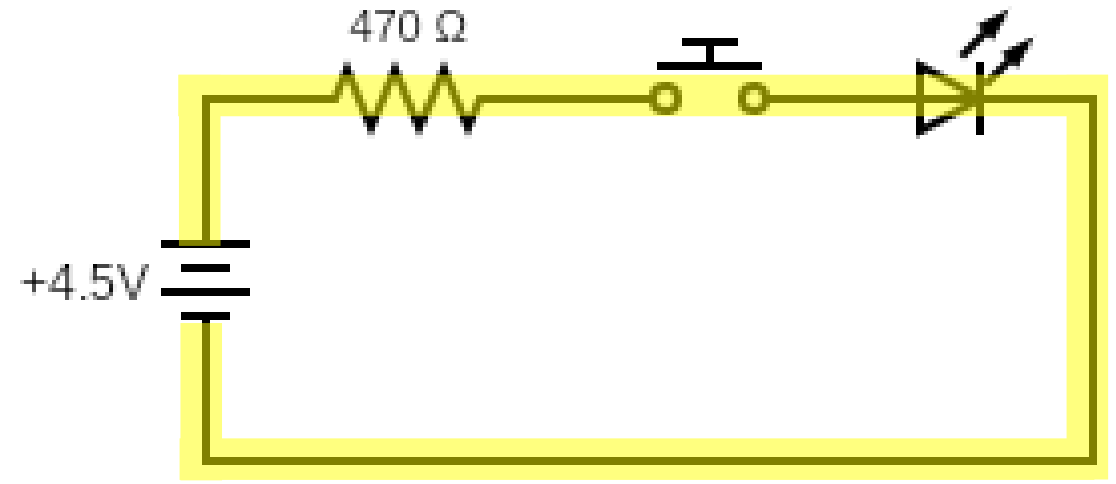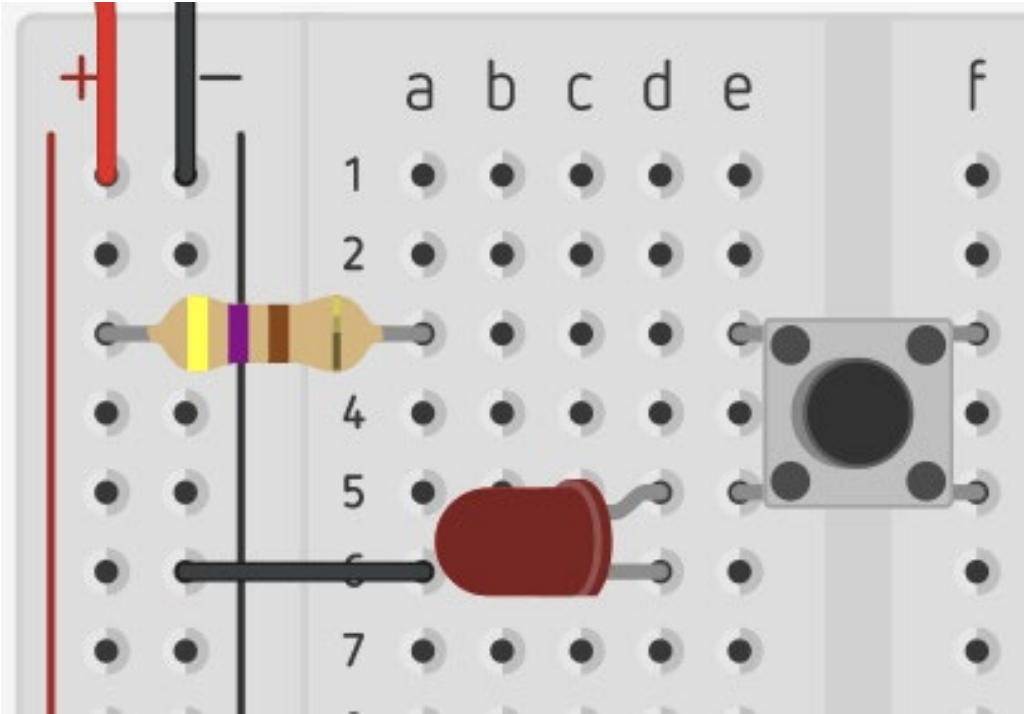Connect the (+)
leg of the LED to
5D and the other
leg (-) to 6D



Connect the LED to ground by connecting one end of the wire to 6A and the other end to the (-) power rail.



Turn the LED on and off using the button switch!

If it doesn't work, check to see if your LED is backwards. Also, check the orientation of the pushbutton switch to make sure connection is made between the same side pins.

SQUARE BRAIN

BASIC LED CIRCUIT
with Button Switch

