

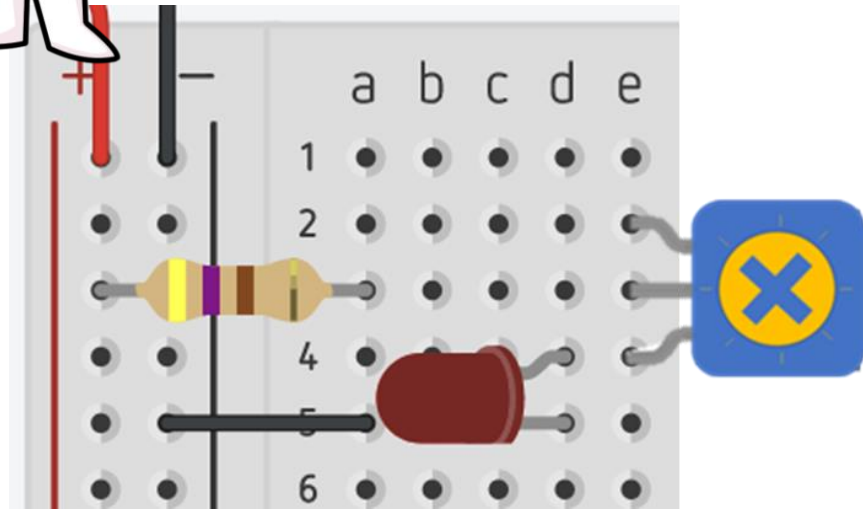
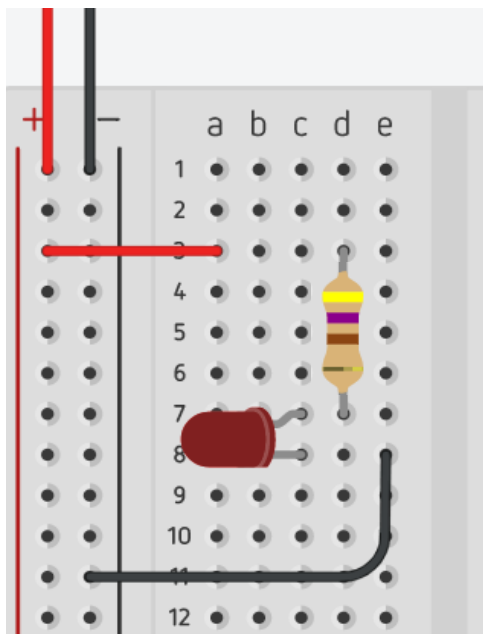


Can You Combine the Circuits Into One!?

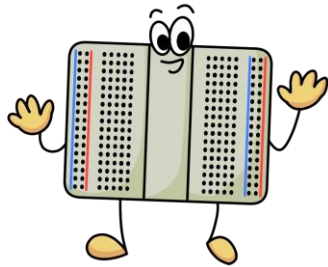How can we create one complex circuit that is a combination of all these simple circuits from Level 1?



YOU GOT THIS!

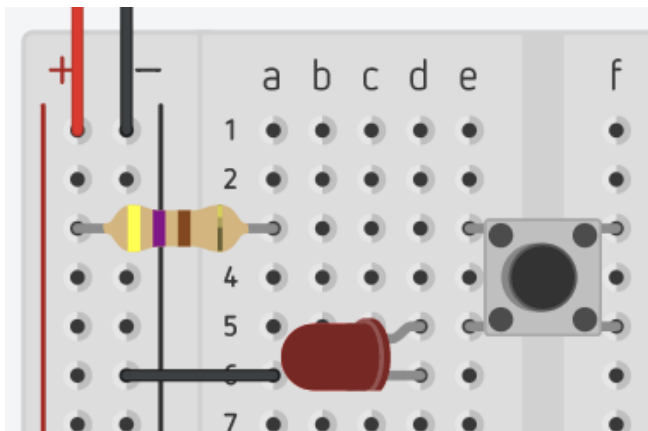

Use a 470Ω resistor, POT, LED, Push Button Switch, breadboard, battery pack, and wires!

