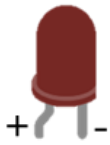


Can You Fix the Circuits?!

The LEDs in each of these circuits will not light up! Please identify and fix the problems so we have circuits with LEDs that light up!



LEDs will not light up if connected backwards

