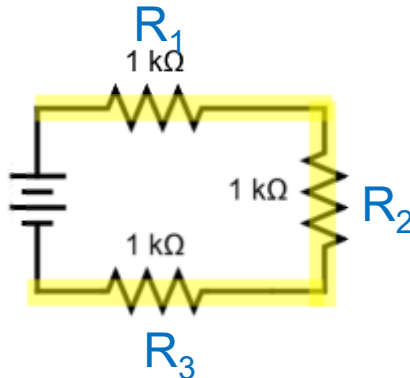


Let's Figure Out the Total Resistance in the Circuits!

Find the total resistance for both
Circuit 1 and **Circuit 2**.

To find the *total resistance* (R_T) in **Circuit 1**, let's find the resistance through R_1 , R_2 and R_3 which are in **series**.




$$R_T = R_1 + R_2 + R_3$$

$$R_T = 1000 + 1000 + 1000$$

$$R_T = 3000\Omega \text{ or } 3K\Omega$$

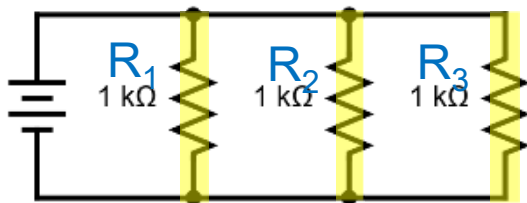To find the *total resistance* (R_T) in **Circuit 2**, let's find the resistance through R_1 , R_2 and R_3 which are in **parallel**.



$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{1000} + \frac{1}{1000} + \frac{1}{1000}$$

$$\frac{1}{R_T} = \frac{3}{1000}$$


$$\frac{1}{R_T} \approx \frac{1}{333.3}$$

$$R_T \approx 333.3\Omega$$




Let's Figure Out the Total Resistance in the Circuits!

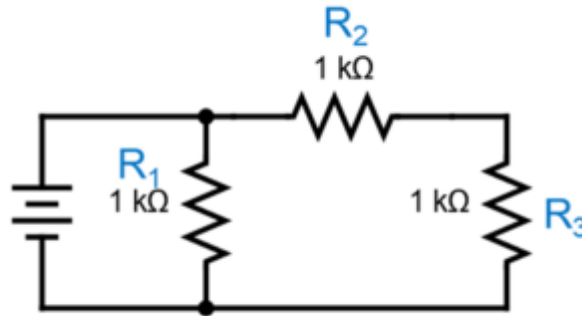Find the total resistance for **Circuit 3** below.





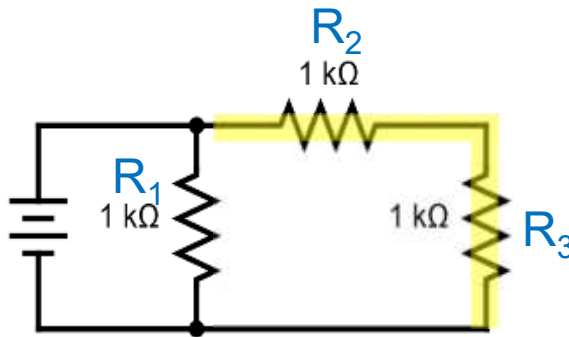To find the *total resistance* (R_T) in **Circuit 3**, let's start by finding the resistance through R_2 and R_3 which are in **series**.



$$\begin{aligned} &= R_2 + R_3 \\ &= 1000 + 1000 \\ &= \mathbf{2000\Omega} \text{ or } \mathbf{2K\Omega} \end{aligned}$$

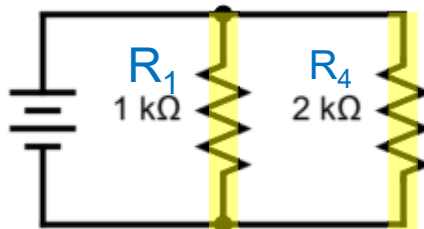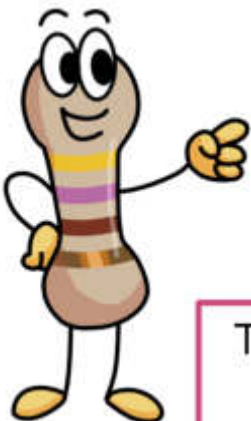Now let's find the resistance between R_2 and R_4 which are in parallel.



The total resistance for **Circuit 3** is approximately **666.7Ω!**

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_4}$$

$$\frac{1}{R_T} = \frac{1}{1000} + \frac{1}{2000}$$


$$\frac{1}{R_T} = \frac{3000}{2,000,000} \approx \frac{1}{666.7}$$

$$\mathbf{R_T \approx 666.7\Omega}$$




Let's Figure Out the Total Resistance in the Circuits!

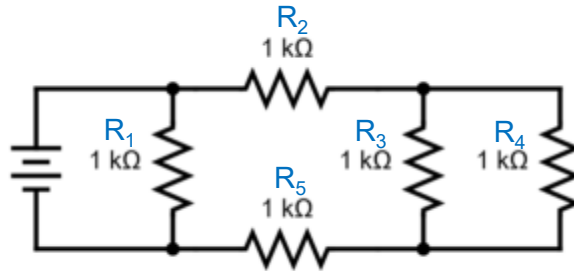Find the total resistance for **Circuit 4** below.



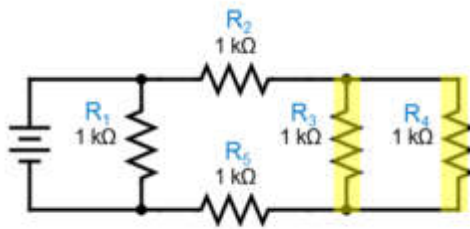To find the *total resistance* (R_T) in **Circuit 4**, let's start by finding the resistance through R_2 and R_4 which are in **parallel**.




$$\frac{1}{R} = \frac{1}{R_3} + \frac{1}{R_4}$$

$$\frac{1}{R} = \frac{1}{1000} + \frac{1}{1000}$$

$$\frac{1}{R} = \frac{2}{1000} = \frac{1}{500}$$

$R = 500\Omega$ $R_5 = 500\Omega$

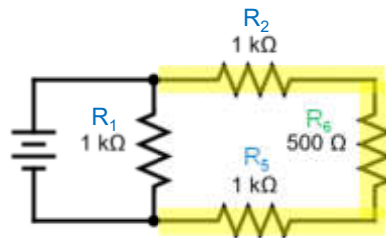Now let's find the resistance between R_2 , R_6 and R_5 which are in **series**.



$$R = R_2 + R_6 + R_5$$


$$R = 1000 + 500 + 1000$$

$$R = 2500\Omega \text{ or } 2.5K\Omega$$

$R_7 = 2500\Omega$

Now let's find the resistance between R_1 and R_7 which are in **parallel**.

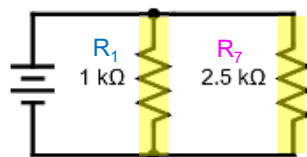The total resistance for **Circuit 4** is approximately **714.3Ω**!




$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_7}$$

$$\frac{1}{R_T} = \frac{1}{1000} + \frac{1}{2500}$$

$$\frac{1}{R_T} = \frac{3500}{2,500,000} \approx \frac{1}{714.3}$$


$R_T = 714.3\Omega$

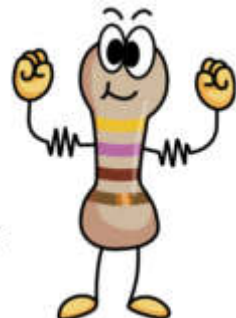


Let's Figure Out the Total Resistance in the Circuits!

SHOW ALL YOUR WORK!

CIRCUIT 1

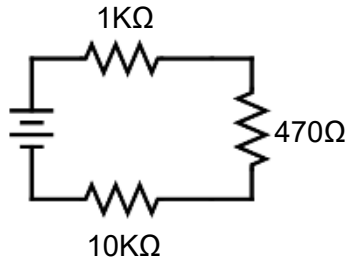

CIRCUIT 2

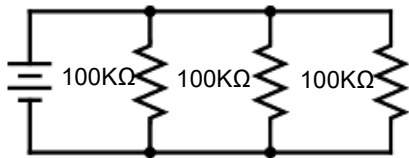

CIRCUIT 3

