
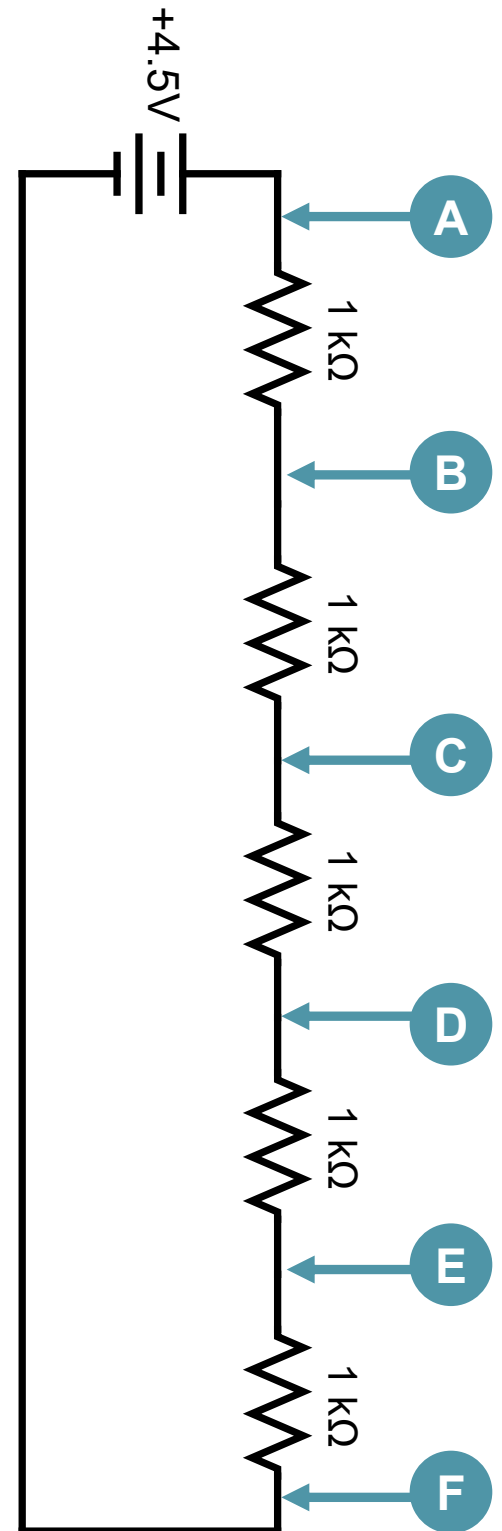


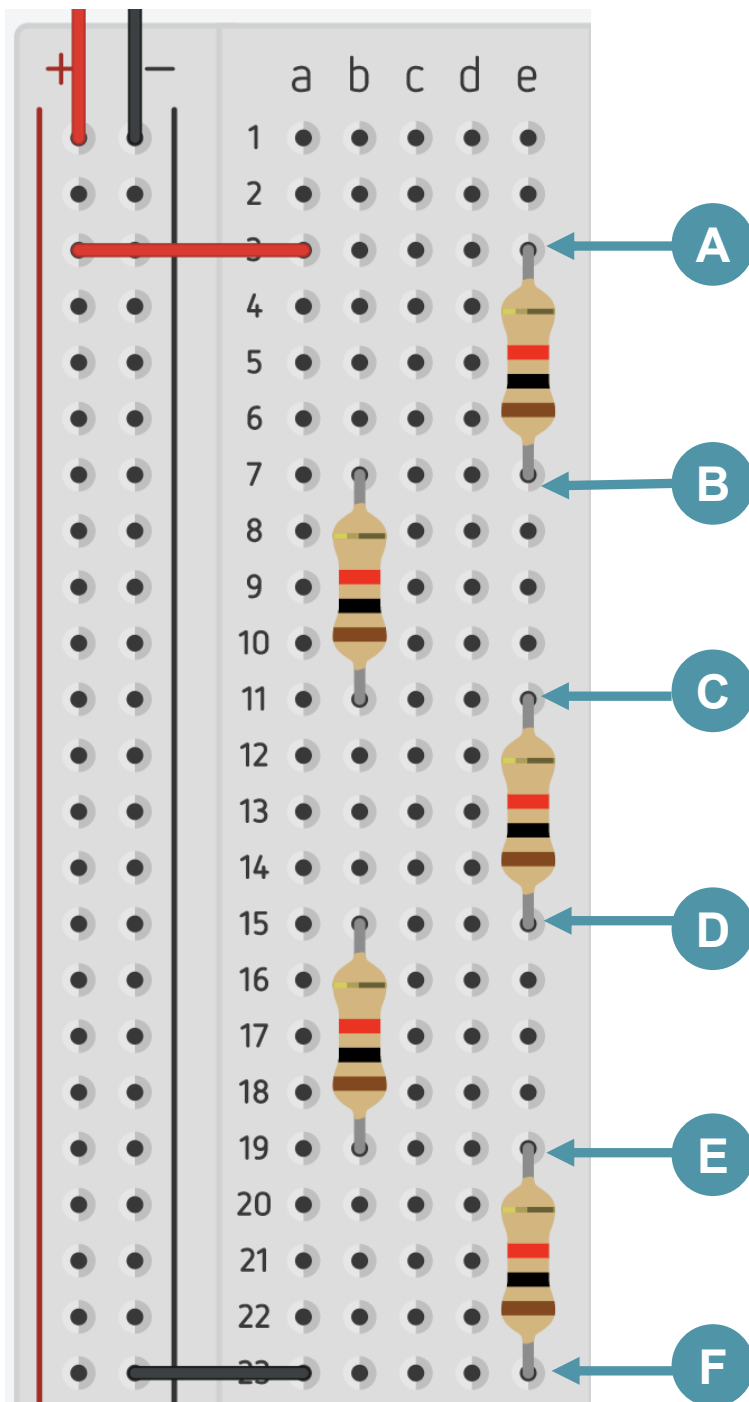
# Measuring Electrical Potential Difference





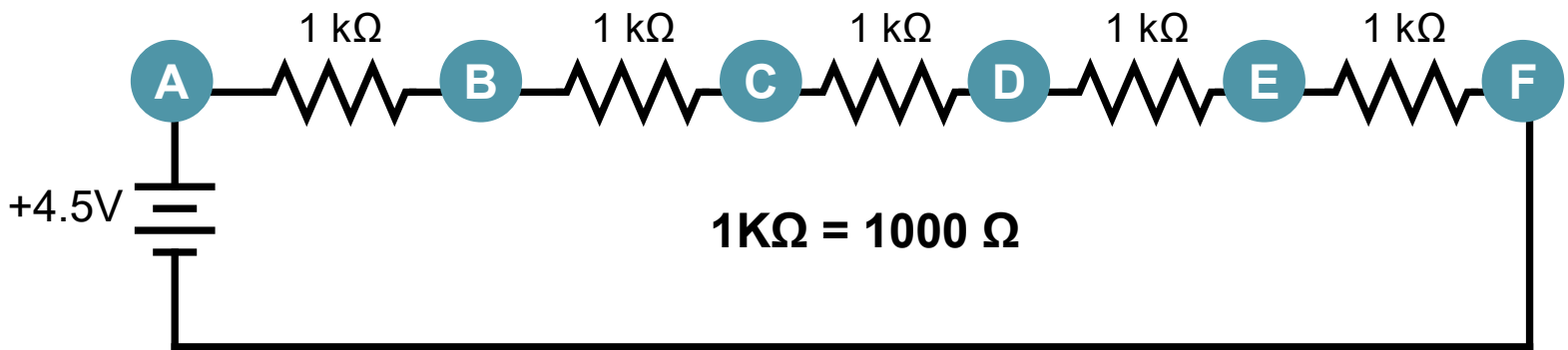
Use the multimeter to measure voltage in the circuit at various places. Record your findings in the data table. What do you notice?



# Measuring Electrical Potential Difference



Red Lead 	Black Lead 	Multimeter Voltage
A	F	
B	F	
C	F	
D	F	
E	F	
F	F	
A	B	
B	C	
C	D	
D	E	

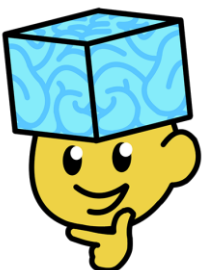

What conclusions can you make based on the measurements you have taken?

