

TRY THIS!

Identify each of the logic gates below and fill in the blank of the output for given the inputs.

